

# Snail Gear Building instructions V1.1

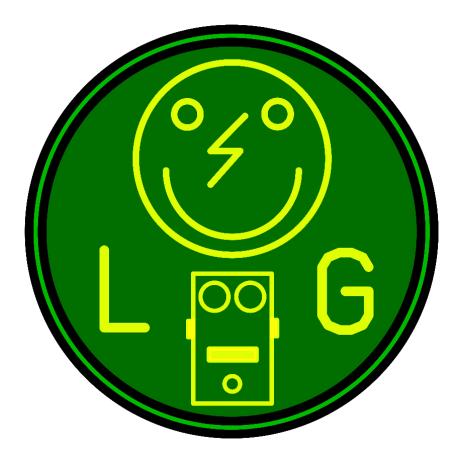

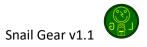




## Table of contents

Components	3
PCB layout	
General guideline for components	
General building tips	5
Modifications	6
Biasing	7
Off board wiring	7
Troubleshooting	8
Schematic	9


Read this <u>entire</u> manual thoroughly before you start to building the effect! Especially the Modification and Biasing part. Decide before building the effect which mods you want to try so that you do not need to desolder parts later.

Last update: 26-02-2017

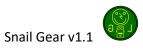



## Components

Name	Value	Comment	Name	Value	Comment
C1	47n	МКТ	R1	1k	
C2	22n	MKT	R2	470k	
С3	1u	Electrolyte	R3	10k	
C4	47u	Electrolyte	R4	22k	
C5	1u	Electrolyte	R5	3k3	
C6	470n	Electrolyte!	R6	470k	
C7	33n	МКТ	R7	47k	
C8	1u	Electrolyte	R8	1M	
С9	22n	МКТ	R9	1M	
C10	1u	Electrolyte	R10	1M	
C11	10u	Electrolyte	R11	10k	
C12	1n	МКТ	R12	1k	
C13	1u	Electrolyte	R13	100k	
C14	1u	Electrolyte	R14	470R	
C15	47n	МКТ	R15	220k	
C16	10u	Electrolyte	R16	390R	
C17	33u	Electrolyte	R17	1M	
C18	10u	Electrolyte	R18	1k	
D1	Zener 5,6V		R19	390k	
D2	1n4148		R20	4k7	
D3	1n4148		R21	4k7	
D4	1n4148		R22	100k	
IC1	TL071		R23	100k	
Q1	BC549C		R24	10k	
Q2	2SK30A	2N5457 use extra D pad	R25	22k	
Q3	BC549C		R26	22k	
Q4	BC549C		R27	1M	
Q5	BC549C	Match with Q6	VR1	A100k	Sensitivity
Q6	BC549C	Match with Q5	VR2	B25k	Attack
			VR3	B10k	BIAS Trim pot

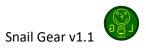

## PCB layout

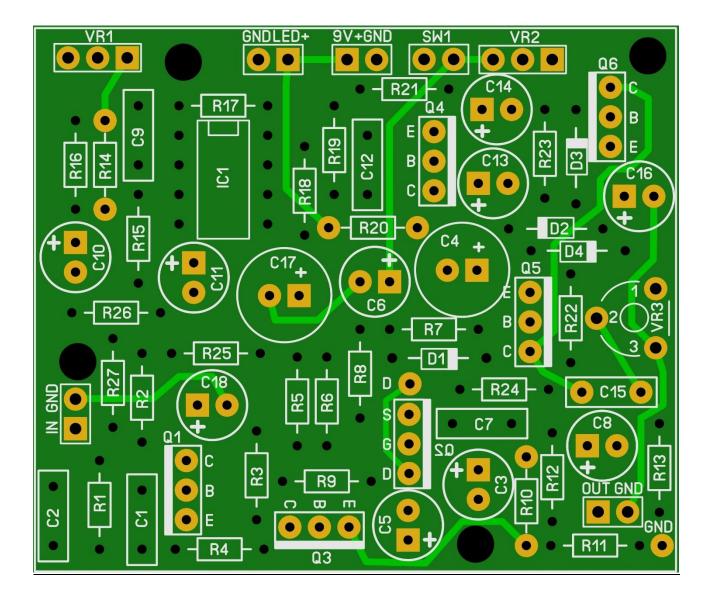

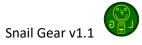



## General guideline for components

- Capacitors: All values under 1nF should be ceramic disks or silver mica. From 1nF up to 1uF should be SMF (Panasonic stacked metal film) or MKT (Metallized plastic polyester) and values over 1uF use electrolyte caps 16V+ rated and watch out for polarity.
- Resistors: use 1% metal film for the best results.
- Socket the IC's. This way you can easily mod them or replace them if they break.
- Orientation of the transistors: the white stripe on the PCB indicates where the flat side of the transistor should be <u>except</u> for Q2, that one the bold side is facing the white stripe.

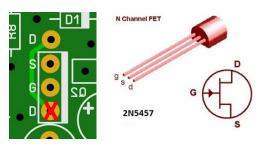
### General building tips

Before you start you will need to make sure that you match the Hfe of Q5 and Q6 for the best result. Matching is done by using a Digital Multi Meter (DMM). Get them as close together as possible. You can use any BC549A/B/C or even BC550A/B/C for Q1,Q3,Q4,Q5 and Q6. For Q2 you can <u>only</u> use a 2SK30A or a 2N5457, but the pinout is different so you'll need to use the extra D pad for the 2N5457:



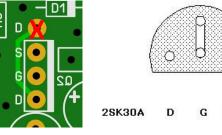

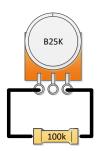The original Attack pot is B20K. You can easily use the readily available B25K or you can place a 100K resistor between pins 1 and 3 to lower the B25K to B20K.



Soldering this board can be very complicated for some people since the solder pads are very close together. Use a magnifying glass to make the job easier. If you want to experiment with other transistors than you could socket them instead of soldering them to the board. You'll need a 20 SIL, break off the sockets and solder them to the board.

Start by soldering D2-D4 and then solder the resistors (but not yet VR3) and then D1.

**Note:** Diodes are fragile!! Do not expose them to heat for too long or they'll break. Do not blow on your solder in an attempt to cool it down. That will possibly result in a bad join that might corrode!

Next, solder the IC sockets, and transistors or if desired the transistor sockets (only if you want to try different transistors!) then the VR3 and MKT. Lastly solder the electrolyte capacitors.


Place the IC (and transistors) and you are almost ready to rock. The flat sides of the transistor are indicated by the thick white line.

Besides the components mentioned in the table on the page 3, you will need:

- **2 input jacks**. 2 mono jacks if you are not going to use a battery but only the 9V adapter. 1 mono (for output) and 1 stereo jack (for input) if you will be using both a 9V battery and the 9V adapter.
- **1x 3PDT footswitch** (9 pins). I also sell an easy off board circuit for true bypass.
- 2,1mm DC jack (isolated).
- 9v battery clip (optional).
- 22 gage stranded hook-up wire.
- 1 x 3mm LED (and if needed a LED holder to mount it in the enclosure)
- Hammond 1590B case (or similar) in your favorite color. A Hammond 1590BB will give you more room to build especially when using the swell mod.
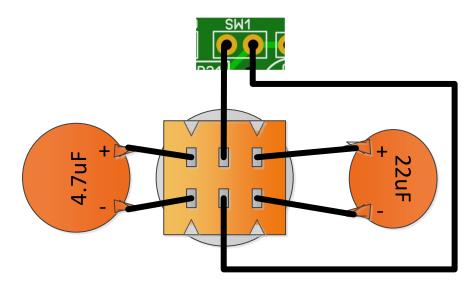
#### **Modifications**

• Swell MOD. You can extend the swell time by changing C6 to a higher value. Especially for this mod the SW1 is added to the board. If you do not decide to use the mod then leave out the SW1. If you do want to use the mod, I suggest using a DP3T (ON/OFF/ON) switch with the 4.7uF on one side and eg. a 22uF on the other side. Experiment with different values before you decide to do the mod. You could even make a rotary switch with even more values! The lower you set the Attack, the longer the swell takes. In combination with a 22uF (C6) it is about 0,5 seconds.



• The original uses a LM741 instead of a TL071.


## **Biasing**

The most important part of this build is the biasing. If your effect is inaudible at low attack settings then it is not biased correctly. Biasing can be done by ear, but can be difficult, so take your time.

- 1. Turn Attack to 0 (=fully counterclockwise) and Sensitivity to 5 (=halfway/12 o'clock) and VR3 to 10 (=fully clockwise)
- 2. Turn the VR3 until you hear the effect swell correct and without volume loss.

NB the Sensitivity pot is used to adapt the effect to the amount of input the effect gets (like an input boost). If you use a booster/fuzz in front of the effect, you will need to lower the Sensitivity to get the optimal result.


## Off board wiring

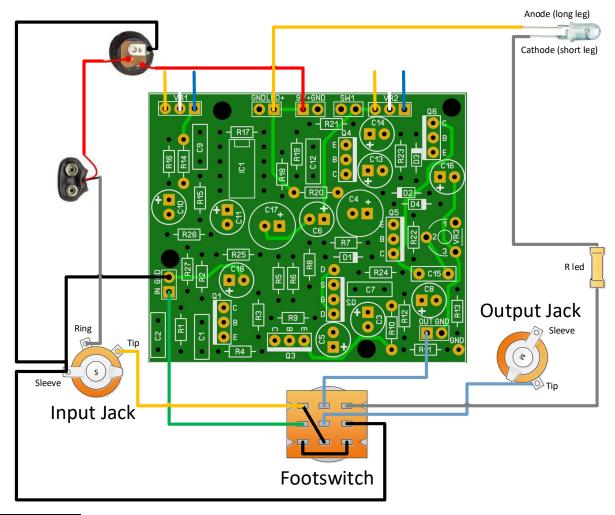



Blue

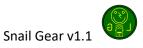= pin 1 The LEDs requires a resistor (R led in the diagram) depending on the White = pin 2type of LED you are using. To be safe use a 3k3 or 4k7 resistor. If Yellow = pin 3you want to be more exact then go here: http://www.muzique.com/schem/led.htm




## Troubleshooting

All PCB's have been 100% factory e-tested and out of every batch I receive I build a effect to double check, so there should not be a connection problem on the PCB itself.

The board is not working (at all), what now?

- Check if your 9V is plugged in correctly (and/or soldered correctly on the board).
- Check that you <u>oriented</u> the capacitors, IC's ,transistors and diodes the right way. SMF, MKT capacitors and resistors do not need to be oriented.
- Check if you used the correct values of the components. For resistors you can look here: http://www.diyaudioandvideo.com/Electronics/Color/
- Double and triple check your soldering! A loose or cold solder can be really bad for your board.
- Replace the IC's and transistors, one might be defective. Before doing that first unplug the 9V and wait 5 seconds.
- Check that you have good/high grade components. A lot of Chinese sourced parts are fakes (especially high end opamps, vintage diodes and transistors) so be careful that you source your parts from reliable suppliers.

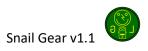

## Schematic

